 


UART DESIGN

By Tylor Cooks

Overview UART



Full UART Module with Parity

Implemented ASM chart.
3 modules implemented and instantiated together.

- Baud Rate Generator
- Receiver
- Transmitter


Implemented logic to combat metastability.

Implemented self-checking testbench



Method order and Goal

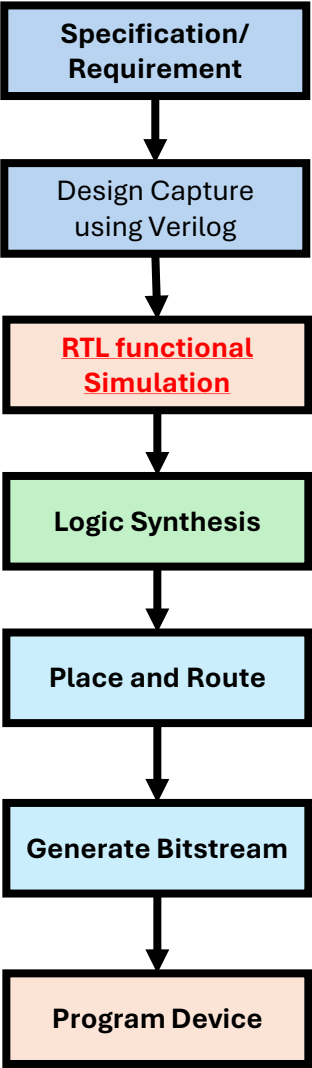Specification/Requirements
Design Capture using Verilog
RTL functional Simulation
Logic Synthesis
Place and Route (Implementation)
Generate Bitstream
Program Device



Specification/Requirements

Baud Generator, Receiver, Transmitter

• Baud Generator


- Requirements/Specifications
 - To generate a sampling signal whose frequency is exactly 16 times the UART's designated baud rate from the system clock.
 - Account for any adjustments needed for an accurate count

• Receiver

- Requirements/Specifications
 - Obtain data at a specific baud rate , oversampled x16
 - Implement false triggering detection, allowing to detect any Start Bit that is less than half-bit time as noise
 - Minimizing **metastability**
 - Implement a parity bit

• Transmitter

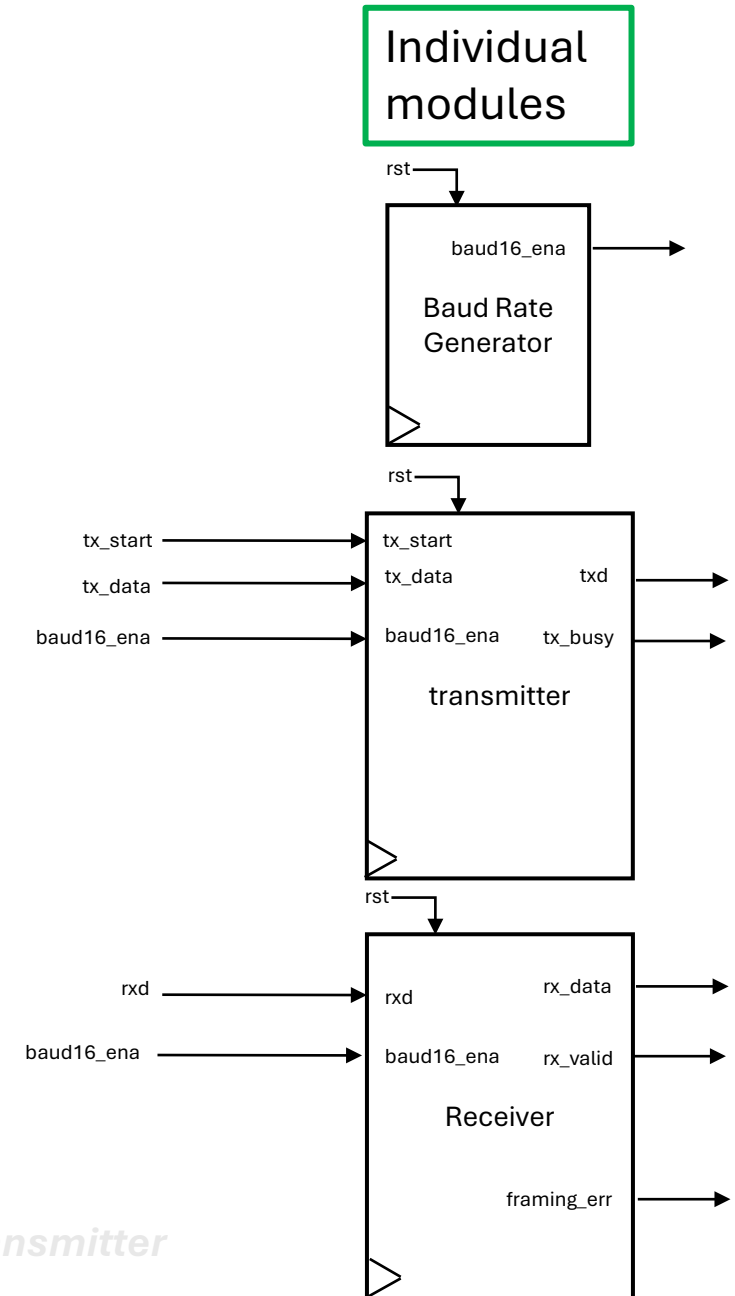- Requirements/Specifications
 - Shift register that loads data in parallel then shifts it out bit by bit at a specific rate(baud rate).
 - A bit is shifted out ,LSB first, every 16 enable ticks.
 - The receiver and transmitter must have the same baud rate as the baud rate generator
 - Implement a parity bit




Key Point – Specification/Requirements of Baud Generator, Receiver, and Transmitter

UART Receiver DESCRIPTION

What is UART Receiver?

- UART (Universal asynchronous receiver and transmitter)
 - Includes a transmitter and receiver
 - **Receiver**
 - Shift register that receives the data at a specific **baud rate** bit by bit via oversampling then reassembles the data.
 - The receiver and transmitter must have the same baud rate → **baud rate generator**
 - States
 - **sIDLE**: Active high(1), held in active high to show that the line and transmitter are not damaged.
 - **sSTART**: Active low(0), to signals the receiver that new data is coming.
 - **sSHIFT**: Receives the incoming data, LSB first, gets held in a shifting register.
 - **sSTOP**: Signals to the receiver that the incoming data is finished.

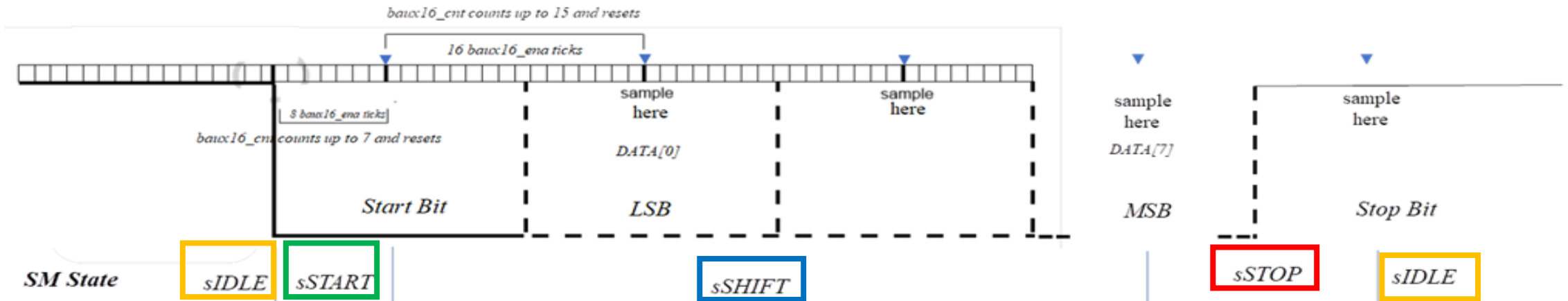

UART Transmitter DESCRIPTION

What is UART Transmitter?

- UART (Universal asynchronous receiver and transmitter)
 - Includes a transmitter and receiver
 - **Transmitter** (The focus of the presentation)
 - Shift register that loads data in **parallel** then shifts it out bit by bit at a specific rate(baud rate).
 - A bit is shifted out ,LSB first, every 16 enable ticks.
 - The receiver and transmitter must have the same baud rate → **baud rate generator**
 - States
 - sIDLE: Active high(1) txd, awaits tx_start signal to load data word.
 - sWAIT: Waits one clock cycle before transitioning to Active Low(0) txd.
 - sSTART: Active low(0) txd, to signal the receiver that new data is coming, transmit first bit(LSB) in the data register.
 - sSHIFT: Transfers the data bit by bit every 16 enable ticks.
 - sSTOP: Transmits and active low(0) txd signal for 1 clock cycle.

Clock Improvement with Fractional Adjustment for Baud Rate Generator

- Without Adjustment (50MHz) 115200 baud rate
 - Rounded Value*
 - Period = $27 \times (20\text{ns}) = \mathbf{540\text{ns}}$
 - Oversampled 16x = $(540\text{ns}) \times 16 = \mathbf{8640\text{ns}}$
 - Real Value*
 - $27.126736 \times (20\text{ns}) \times 16 = \sim \mathbf{8680\text{ns}}$
 - Absolute error*
 - $8680\text{ns} - 8640\text{ns} = \mathbf{40\text{ns}}$ (A difference of 40ns)
- With Adjustment (baudx16_ena period is extended by one 50MHz (20ns) clock every 8th baudx16_ena)
 - Oversampled adjusted value*
 - $14 \times (27 \times 20\text{ns}) + 2(28 \times 20\text{ns}) = \mathbf{8680\text{ns}}$
 - Absolute error*
 - $8680\text{ns} - 8680\text{ns} = \sim 0$
 - The Error bit-time is near zero*

Every 8th time the baud generator sends a pulse, it has one extra to adjust the clock for the baud rate

Fractional Adjustment	Common Baud rates bits/second
1/8 = 0.125	115200: 27.126
2/8 = 0.250	57600: 55.253
3/8 = 0.375	38400: 81.380
4/8 = 0.500	28800: 108.507
5/8 = 0.625	230400: 13.563
6/8 = 0.750	19200: 162.760

(System clock) divided by (desired baud rate)

UART Instantiation

Structural Description

- Module instantiation of UART

- Sharing the same baud rate generator
- txd → rxd
- Purpose:
 - Combining individual modules into one.

- Variables:

- rst**: resets the circuit
- baud16_ena**: sends a pulse every 16 count, responsible for the baud rate
- tx_start** receives a 1-clock-wide pulse to initiate transmission
- tx_data**: receives the data being transmitted
- txd**: output of the transmitter, sends data serially to the receiver
- tx_busy**: no new data for the input of the transmitter if high, only accepts new data when low.
- rxd**: receives bits
- rx_data**: outputs the 8 data bits
- rx_valid**: UART received data valid
- framing_err**: for a framing error

```
input sysclk, rst,
input tx_start,
input parity_en, odd_even,
input [DBIT-1:0] tx_data,
output tx_busy,
output [DBIT-1:0] rx_data,
output rx_valid, framing_err, parity_err
);

wire baudx16_ena;
wire txd;


baudRate_gen2 #(.MOD(MOD)) baudRate_gen
(.sysclk(sysclk), .rst(rst), .baudx16_ena(baudx16_ena));

transmitter #(.DBIT(DBIT), .STOP_B(STOP_B)) transmitter
(.sysclk(sysclk), .rst(rst), .baudx16_ena(baudx16_ena), .tx_start(tx_start), .parity_en(parity_en), .odd_even(odd_even),
.tx_data(tx_data), .txd(txd), .tx_busy(tx_busy));

receiver #(.DBIT(DBIT), .STOP_B(STOP_B)) receiver
(.sysclk(sysclk), .rst(rst), .baudx16_ena(baudx16_ena), .rx_data(rx_data), .parity_en(parity_en), .odd_even(odd_even),
.rxd(txd), .rx_valid(rx_valid), .framing_err(framing_err), .parity_err(parity_err));
endmodule
```

Shows how the two modules are connected, txd to rxd

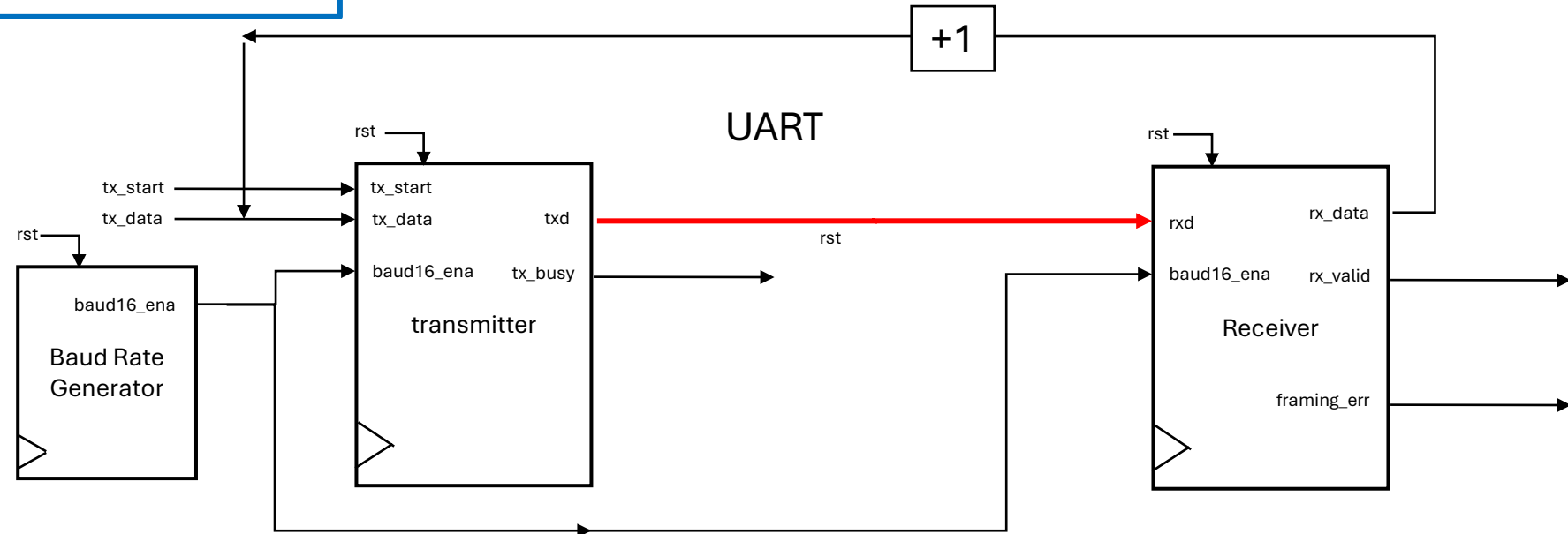Circuit for loop back test for UART module, used in the test bench



Key Point – UART Instantiation

Metastability

Brief overview



• Characteristics

- A probabilistic phenomenon (random future events)
 - Can not build a bit-stable device that cannot go into a metastable state
- Occurs when two asynchronous signals combine such that their resulting output goes into an indeterminate state
- Can remain in a metastable state for an indeterminant amount of time.
 - **Exponentially decreasing function, it will stay in the metastable state.**

• Solution

- D-type Flip Flop in series, on the same system clock.
- Increases the amount of time for the meta-state to be resolved
- Minimizes the probability that the metastability entering the main part of the circuit.

Key Point - Metastability

  

Note: in this design rxd_q[] represents the synchronizer

Block Diagram of parity_bit

Block diagram, Truth table


- **odd_even** decides if the **parity_bit** is going to be calculated with an odd or even configuration.
 - **parity_bit** will be a 1 or 0 depending on the amount of data bits
 - **odd_even** = 0: even parity (keep an even number of 1's)
 - **odd_even** = 1: odd parity (keep an odd number of 1's)
- Calculated the same with transmitter(thr[0]) or receiver (rx_d_q[1])
- **Purpose**
 - Adding a parity bit is a form of error detection. Compares the parity from the receiver and transmitter. If they are both the same, no error, if they are different an error has occurred.

Data (4)bits	Even	Odd
0	0	1
1	0	1
1	1	0
0	0	1
	0	1

• Even number of 1's

Parity bit:

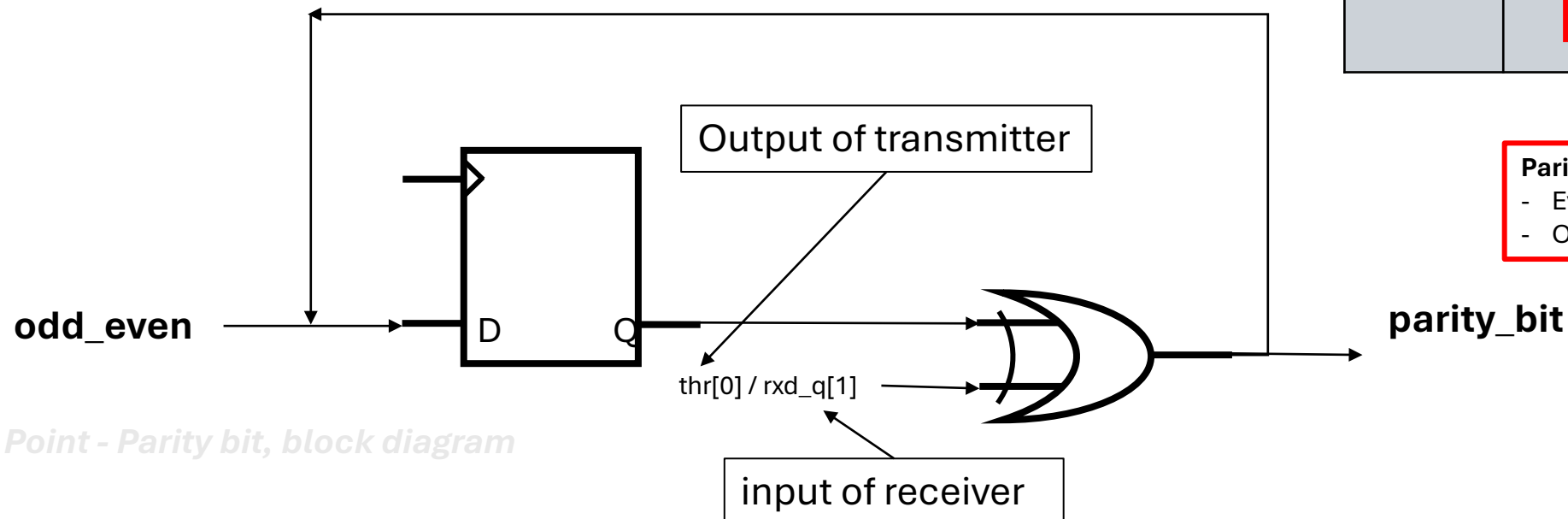- Even : parity bit ← 0
- Odd : parity bit ← 1




Key Point - Parity bit, block diagram

ASM CHART RECEIVER


STATES: sIDLE, sSTART, sSHIFT, sSTOP

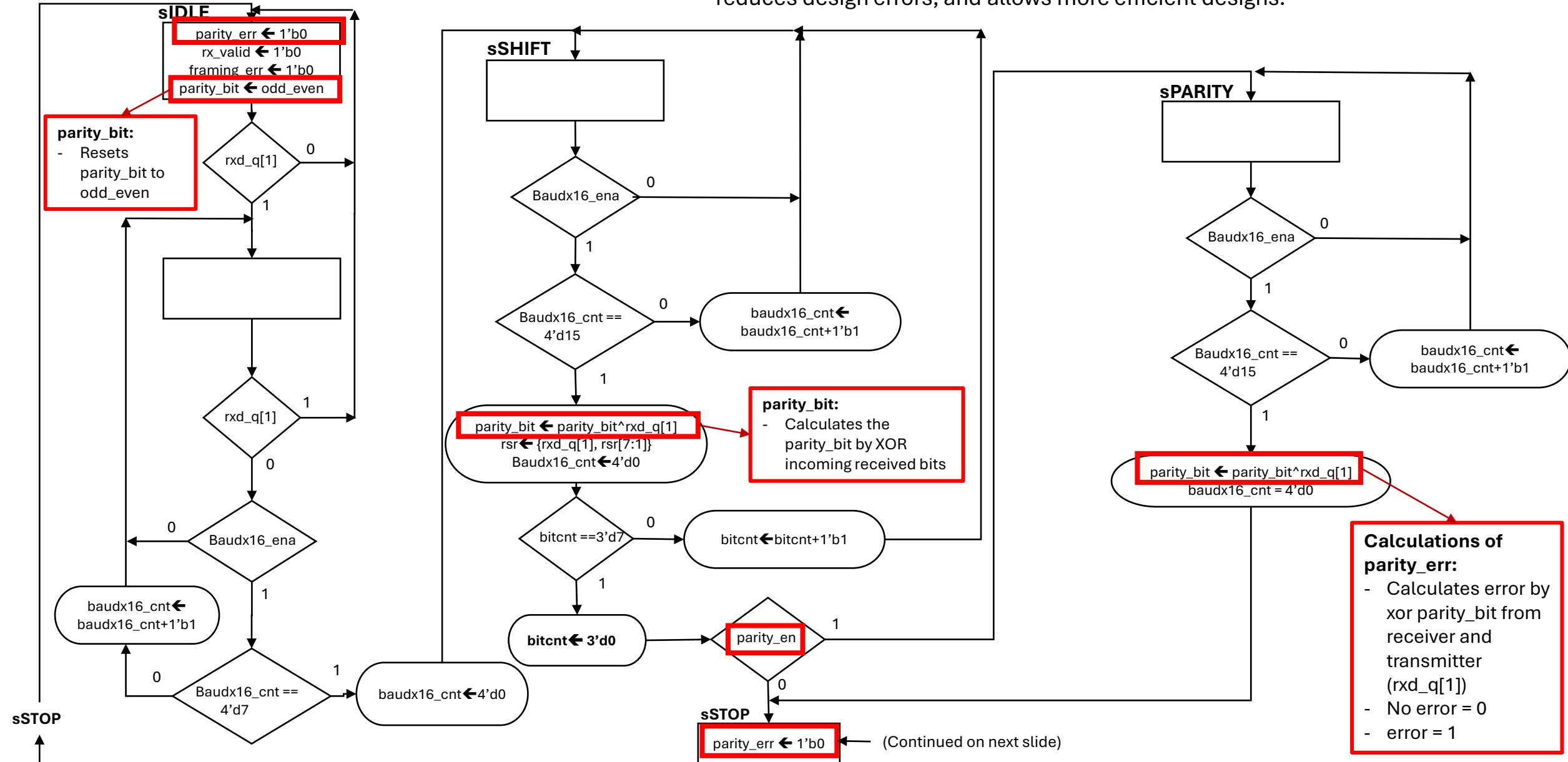Purpose: The ASM chart is part of the design methodology used. A powerful tool that makes easy to understand the operation of a digital system represented by an ASM chart, self-documenting, reduces design errors, and allows more efficient designs.




(Continued on previous slide)

ASM CHART: RECIEVER cont.

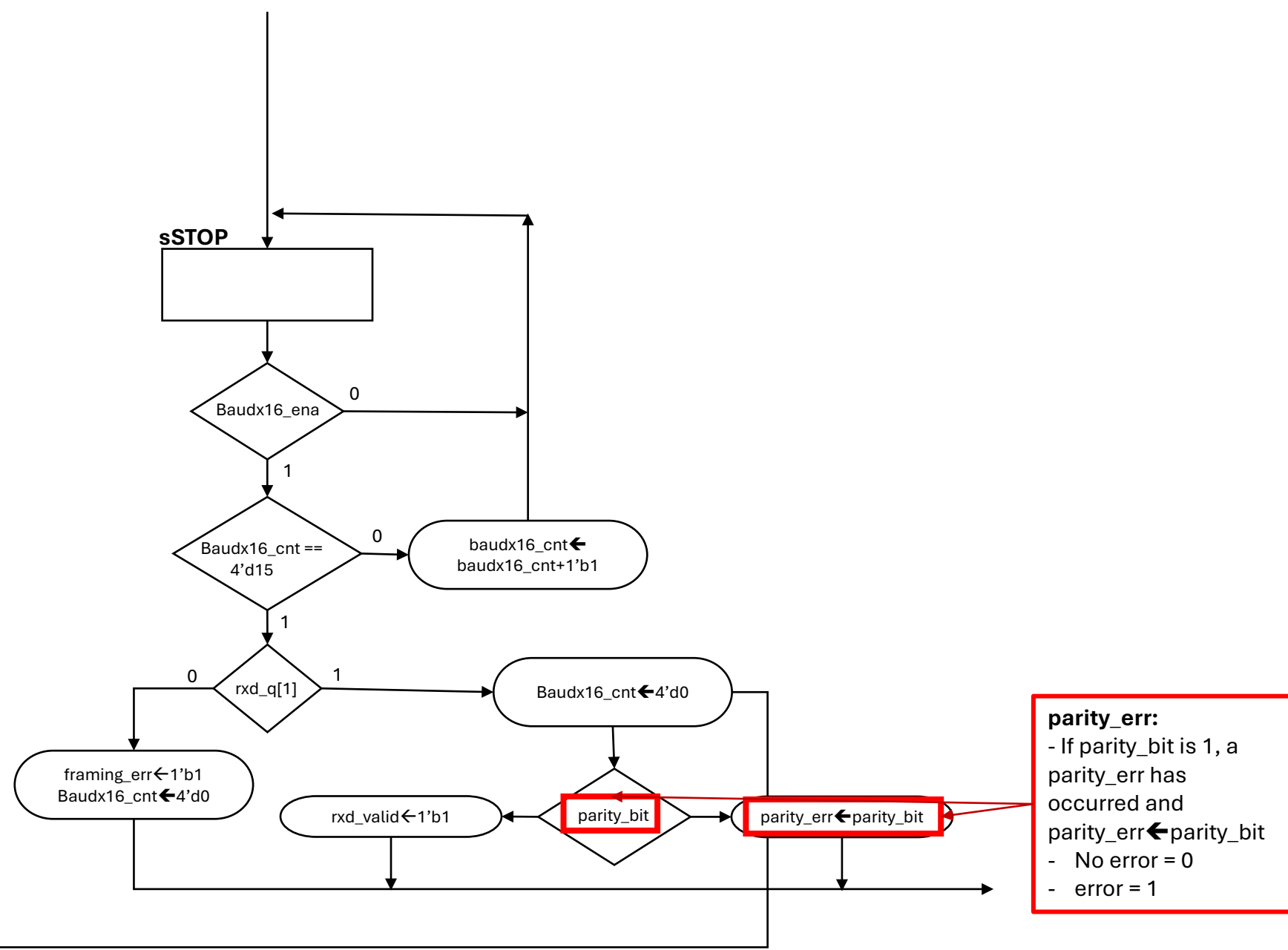


ASM CHART Transmitter

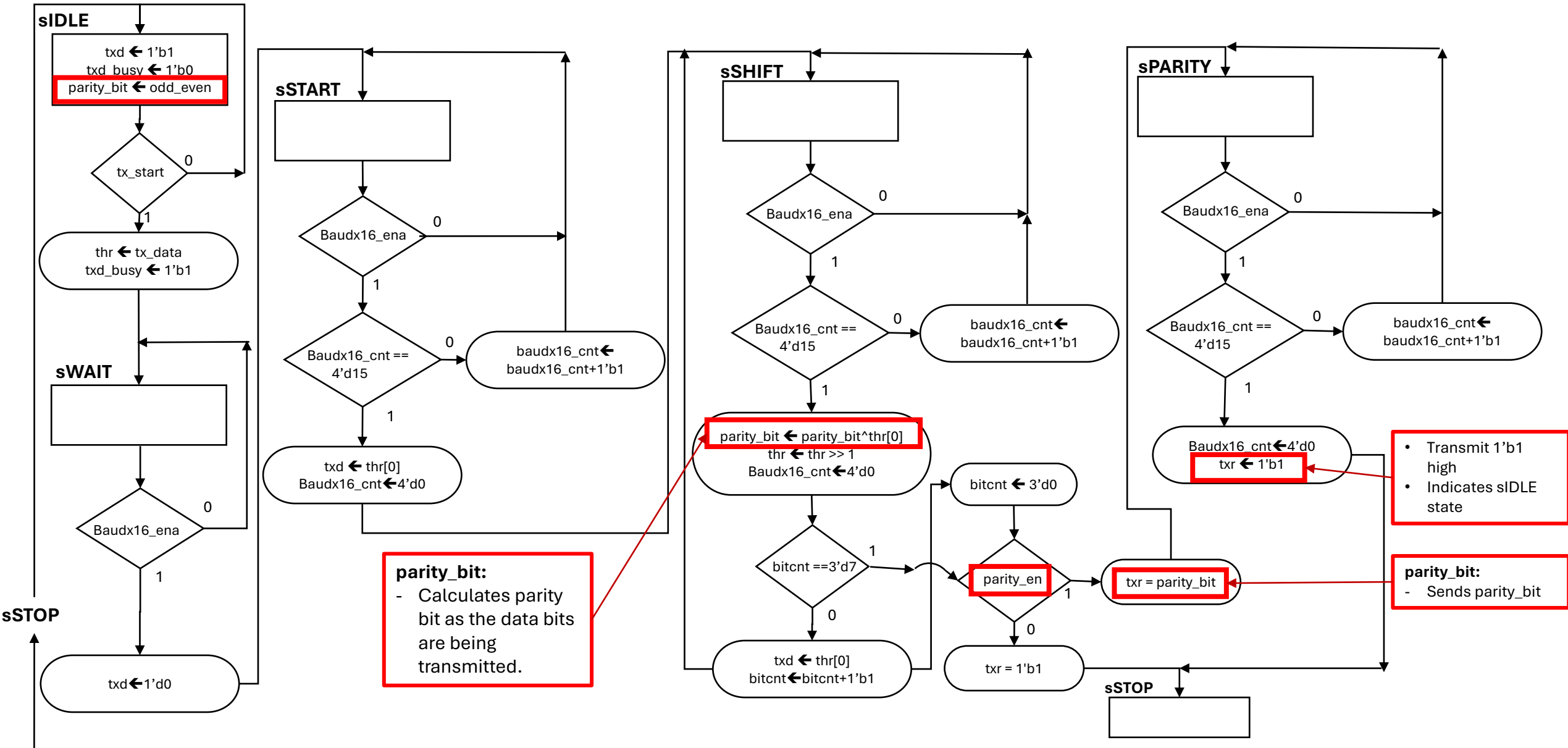STATES: sIDLE, sWAIT, sSTART, sSHIFT, sPARITY, sSTOP



(Continued on previous slide)

ASM CHART: TRANSMITTER cont.

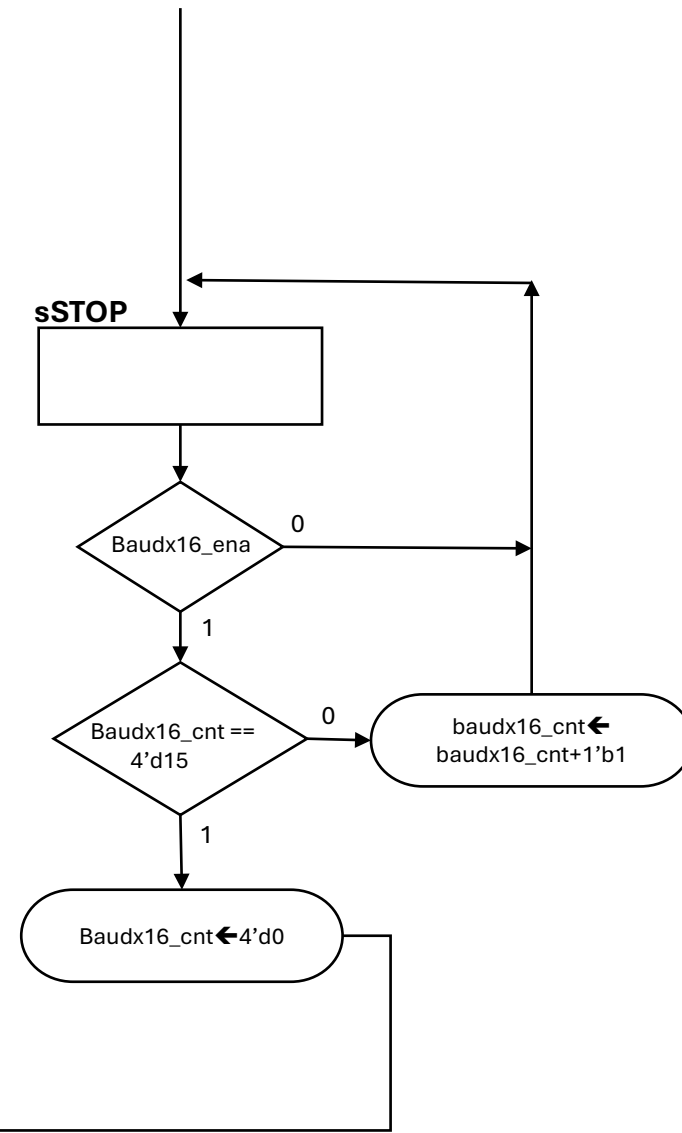

SELF-CHECKING LOOP BACK TESTBENCH

Iterative

```
task sw_test;
integer i, j;
begin
    i = 0;
    j = 0;
    for(i=0; i<255; i=i+1)
    begin
        UART_READ(rx_data+1);
        #(CLK_BIT_PERIOD*12);
        if((tx_data)==rx_data)
            $display(" Received! Input to transmitter = 0x%0h, Output of reciever = 0x%0h",tx_data,(rx_data));
        else
            begin
                $display(" Not Received! Input to transmitter = 0x%0h, Output of reciever = 0x%0h",tx_data,(rx_data));
                j = j+1;
            end
        end
    end

    $display(" Errors counted %0d out of %0d test cycles",j,i);
end
endtask
```

Iterating through 0-255

A Task that sends data to the transmitter

```
task UART_READ;
input [DBITS-1:0] data;
begin
    tx_start = 1'b1;
    tx_data = data;
    #T;
    tx_start = 1'b0;
end
endtask
```

Purpose: the self-checking loop back test sends data from the receiver back to transmitter while iterating through all possible combinations for 8-bits, 255 not counting 0, different values. The Self-checking happens by an output in the terminal, letting the user know if the data is received and how many errors if any.


End portion of the test, iterating 0xf3 → 0xff

```
Received! Input to transmitter = 0xf3, Output of reciever = 0xf3
Received! Input to transmitter = 0xf4, Output of reciever = 0xf4
Received! Input to transmitter = 0xf5, Output of reciever = 0xf5
Received! Input to transmitter = 0xf6, Output of reciever = 0xf6
Received! Input to transmitter = 0xf7, Output of reciever = 0xf7
Received! Input to transmitter = 0xf8, Output of reciever = 0xf8
Received! Input to transmitter = 0xf9, Output of reciever = 0xf9
Received! Input to transmitter = 0xfa, Output of reciever = 0xfa
Received! Input to transmitter = 0xfb, Output of reciever = 0xfb
Received! Input to transmitter = 0xfc, Output of reciever = 0xfc
Received! Input to transmitter = 0xfd, Output of reciever = 0xfd
Received! Input to transmitter = 0xfe, Output of reciever = 0xfe
Received! Input to transmitter = 0xff, Output of reciever = 0xff
Errors counted 0 out of 255 test cycles
```

No errors out of 255 test cycles

Self-Checking Loop Back Test Waveform: ODD PARITY

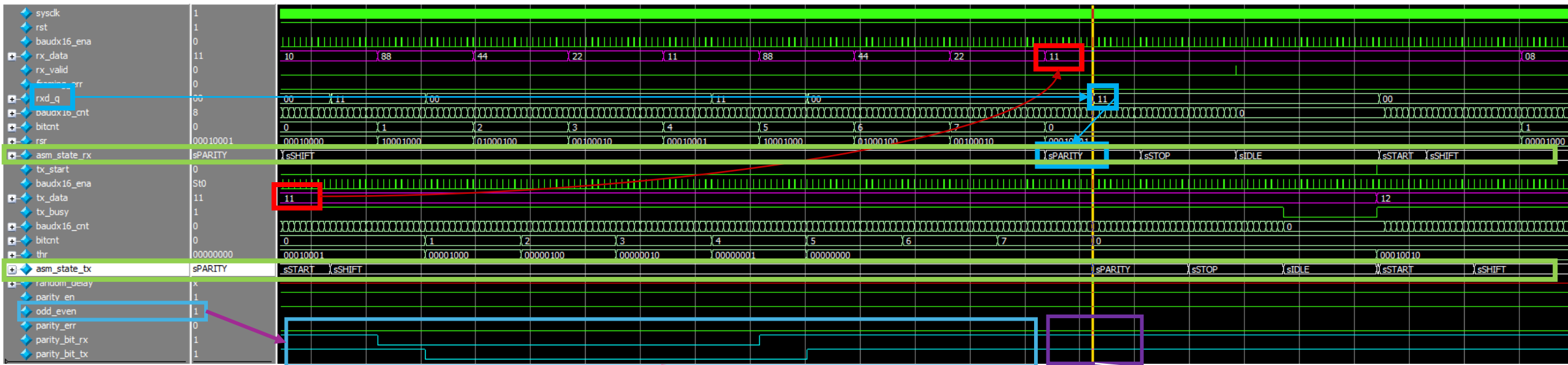Iterative, Full Wave Form, parity_en = 1 , odd_even = 1



The input to the transmitter and output of the receiver

- tx_data (Bottom)
- rx_data (Top)

Transmitter(bottom) States:

- sIDLE
- sWAIT
- sSTART
- sSHIFT
- sPARITY
- sSTOP

Receiver(top) States:

- sIDLE
- sSTART
- sSHIFT
- sPARITY
- sSTOP

- parity_bit calculations

- parity_bit $\leftarrow 1$

Description: shoes the wave form for when the **parity_en = 1** and has an **odd** configuration. The results are that the circuit is working just as expected


Calculated parity_err

- **parity_err** $\leftarrow 0$
- **parity_bit** $\leftarrow 1$
- 0x11 should have **1** parity bit for **odd** configuration.

Synchronizer received bit, rxd_q = 11, which is expected with an **odd** parity configuration

Self-Checking Loop Back Test Waveform: ODD PARITY ERROR TEST

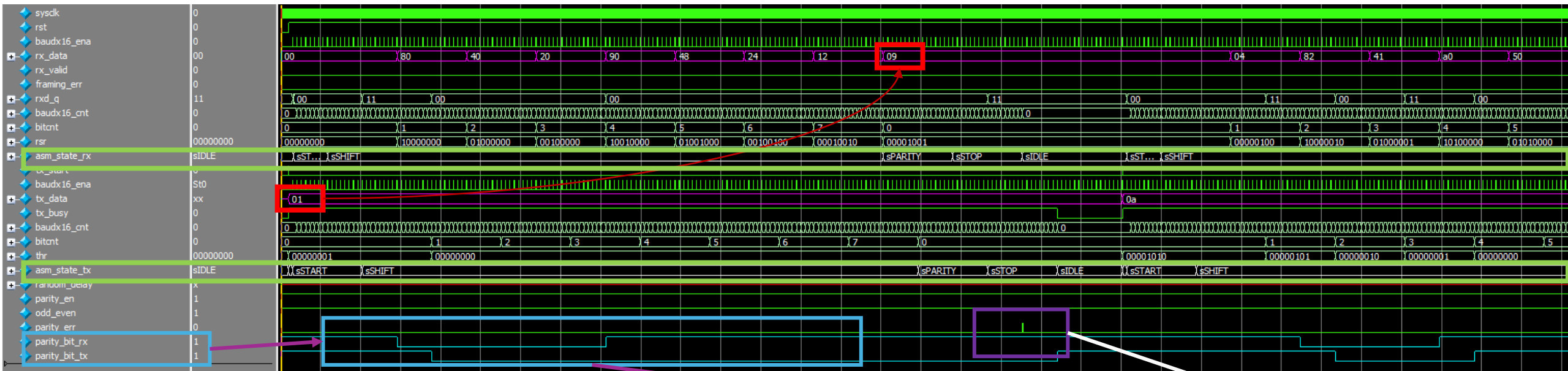Iterative, Full Wave Form, parity_en = 1 , odd_even = 1



The **input** to the transmitter and **output** of the receiver

- tx_data (Bottom)
- rx_data (Top)

• Receiver(top) States:

- sIDLE
- sSTART
- sSHIFT
- sPARITY
- sSTOP

- parity_bit calculations
- parity_bit \leftarrow 1 (error)

Description: shows the wave form for when the **parity_en = 1** and has an **odd** configuration. An **error** is purposely put in the design to show that the **parity_err** will pulse. Everything in the circuit is working as expected


• Transmitter(bottom) States:

- sIDLE
- sWAIT
- sSTART
- sSHIFT
- sPARITY
- sSTOP

- Calculated parity_err
 - **parity_err** \leftarrow 1 for 1 pulse.
- **parity_bit** \leftarrow 1 (error)
 - 0x01 should have **0** parity bit for **Odd** configuration.
- If parity_bit \leftarrow 1 , then rx_valid \leftarrow 0

Self-Checking Loop Back Test Waveform: parity_en ← 0

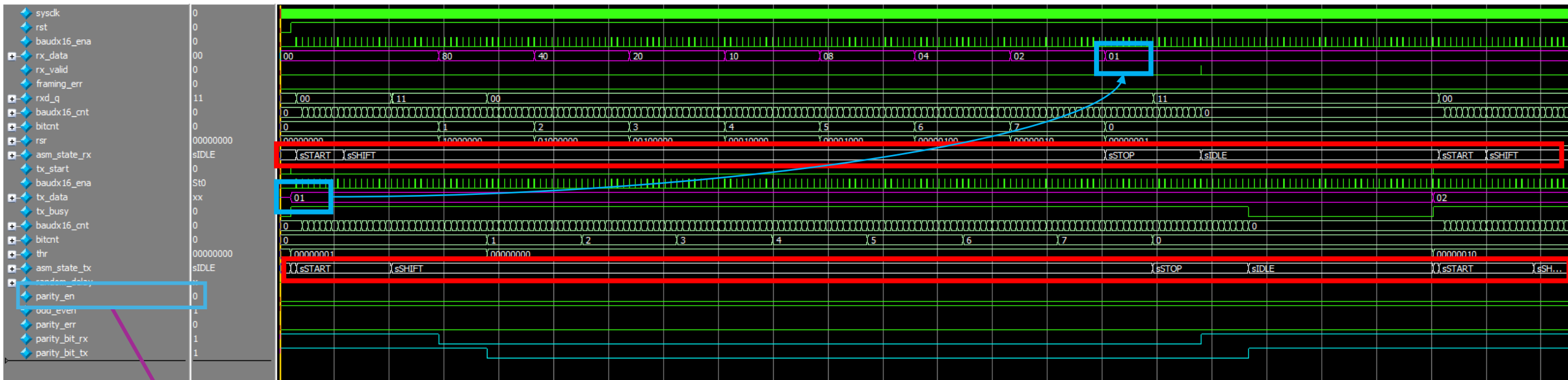Iterative, Full Wave Form, parity_en = 0 , odd_even = 1



- parity_en ← 0

Receiver(top) States:

- sIDLE
- sSTART
- sSHIFT
- sSTOP

Transmitter(bottom) States:

- sIDLE
- sWAIT
- sSTART
- sSHIFT
- sSTOP

The input to the transmitter and output of the receiver

- tx_data (Bottom)
- rx_data (Top)

description:

- With parity_en ← 0, skips the sPARITY state completely for both the transmitter and receiver.
- Still calculates parity_bit but the transmitter doesn't send the parity_bit.